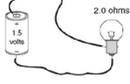


# Series Circuits


Mr. Sudbury

## Circuits

- ▶ A **circuit** is a complete path along which charge can *flow*.
- ▶ Must have a **voltage** (AKA potential difference) to *push the charge*.
- ▶ Circuits can have objects that resist flow of current.
- ▶ For charge to flow- circuit must be *closed*.
- ▶ Ohm's Law is followed in circuits.


$$I = \frac{V}{R}$$


▶ What is the current in this circuit?
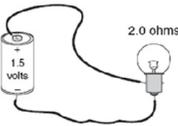
$$I = \frac{V}{R}$$

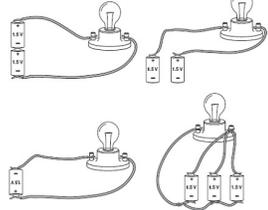
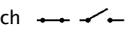
## Circuit


- ▶ Will the bulb light?
  - Circuits must provide a complete path for the charge to flow.



## Schematic Diagrams

Use symbols to represent parts of a circuit.

- Conductor (wire) ———
- Cell —|—
- Batteries (2+ cells) —||—
- Light bulb 
- Open or closed switch 
- Misc. Resistor 

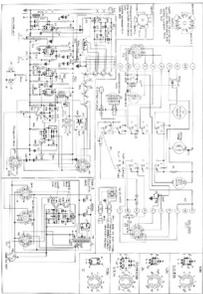

## Types of Circuits

### Series Circuit

- ▶ Single pathway for electrons (charge) to flow between the terminals of the battery or wall socket




### Parallel Circuit

- ▶ Multiple branches (or separate paths) for the flow of electrons (charge).


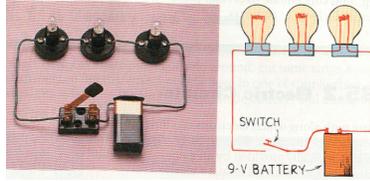
### Series Circuit

- ▶ One path for current to travel.
- ▶ If 1 bulb burns out, **current cannot flow.**



### Series Circuit Rules


1. Single pathway for the current in the circuit. The current throughout the circuit is the constant.
2. Total resistance ( $R_T$ ) is the sum of all the resistors.  
 $R_T = R_1 + R_2 + R_3...$
3. Ohm's law:  $I = \frac{V}{R}$
4. The Voltage is reduced as it goes through each device. Called Voltage drop.  $V = IR$
5. Total voltage ( $V_T$ ) in the circuit must equal the sum of all the voltage drops. (Voltage will be zero back at the battery.)

### Solving Series Circuits
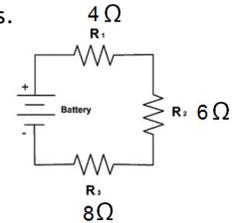
### Resistance in Series Circuits

What is the  $R_T$  in the circuit?


- ▶ The resistance in a series circuit is the sum of all the resistors.
- ▶  $R_T = R_1 + R_2 + R_3 + ...$
- ▶  $R_T = 4\Omega + 6\Omega + 8\Omega =$



### Series Circuits & Ohms Law

- ▶ Circuits follow Ohm's law:
- ▶ If the voltage is 24v, what is the current?


$$I = \frac{V}{R}$$

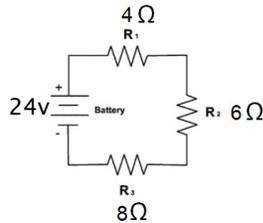
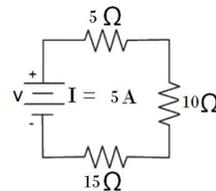
### Series Circuit

$$I = \frac{V}{R} \quad V = IR \quad R = \frac{V}{I}$$


- ▶ What is the  $R_T$ ?
- ▶ What is the voltage drop @ each resistor?
- ▶ What is the  $V_T$ ?


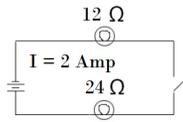
### Series Circuit

$I = \frac{V}{R}$     $V = IR$     $R = \frac{V}{I}$


- ▶ What is the  $R_T$ ?
- ▶ What is the  $V_T$ ?
- ▶ What is the voltage drop @ each resistor?


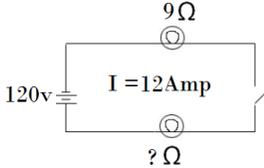
### Series Circuits

$I = \frac{V}{R}$     $V = IR$     $R = \frac{V}{I}$

- ▶ What is the  $R_T$ ?
- ▶ What is the resistance of the unknown resistor?



### The End

- ▶ Series Circuits
  - One path for current to flow.
  - Voltage drops through each resistor and is 0 at the battery.
  - Current travels throughout the circuit.
  - Resistance is added to find total.

